

Using Laplace Transform: (Lab: 34/p: Q4c)
(Tut Q4B/Q4A)

$$X(s) = LC[s^2 y(s) - sy(0) - \dot{y}(0)]$$

$$+ RC[sy(s) - y(0)]$$

$$+ Y(s)$$

$$\therefore Y(s)[s^2 LC + RCs + 1]$$

$$- sy(0)LC - LC\dot{y}(0) - y(0)RC = \underbrace{X(s)}_{\text{due to input}}$$

due to initial conditions

÷ Left/Right by LC.

$$Y(s)\left[s^2 + \frac{RC}{LC}s + \frac{1}{LC}\right]$$

$$= \frac{X(s)}{LC} + sy(0) - \cancel{\frac{X}{LC}}\dot{y}(0) - y(0)\frac{RC}{LC}$$

$$\therefore Y(s) = \frac{1}{\left(s^2 + \frac{R}{L}s + \frac{1}{LC}\right)} \left[\frac{X(s)}{LC} + sy(0) + \dot{y}(0) + \frac{R}{L}y(0) \right]$$

$$\text{sub: } y(0) = 1.5V.$$

$$\dot{y}(0) \Rightarrow \frac{dy(t)}{dt}; \text{ from } i(t) = C \frac{dy(t)}{dt}$$

$$\text{at } i(t=0) = 2A, \therefore i(0) = 2 = C \frac{dy(t)}{dt}$$

$$\Rightarrow \frac{dy(0)}{dt} = \frac{2}{C} = \frac{2}{(6)}$$


$$\dot{y}(0) = 12$$

$$\text{and } X(s) = 0$$

$$\therefore Y(s) = \left[\frac{1}{s^2 + \frac{5}{1}s + \frac{1}{(6)}} \right] \left[\frac{0}{LC} + s \underset{\substack{\uparrow \\ y(0)}}{1.5} + \underset{\substack{\uparrow \\ \dot{y}(0)}}{12} + \frac{5}{1} \underset{\substack{\uparrow \\ y(0)}}{1.5} \right]$$

$$= \left[\frac{1}{s^2 + 5s + 6} \right] [1.5s + 19.5]$$

Tut 4B/
Q 4A

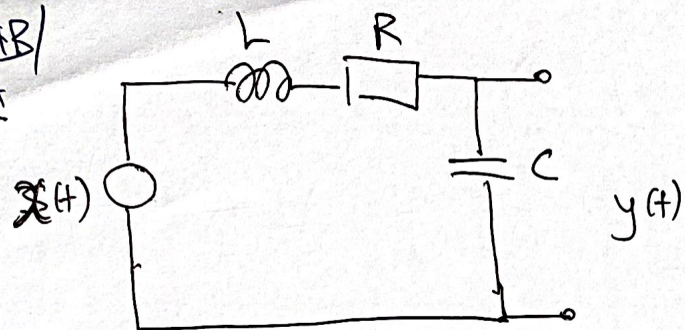

Find $y(t)$, given $L=1$, $R=5$, $C=1/6$ F

at $t=0$, $i(0) = 2$ A
 $y(0) = 1.5$ V. } \Rightarrow initial condition is not relax!

Key idea: a) KVL = sum of voltage = 0.

b) voltage across inductor = $L \frac{di(t)}{dt}$ (change of current across inductor).

voltage across resistor = $i(t) R$

relationship of current across capacitor $\Rightarrow i(t) = C \frac{dy(t)}{dt}$ (change of voltage across capacitor).

Voltage across capacitor $\hat{=} \frac{1}{C} \int i(t) dt$.

① KVL

$$x(t) = V_L + V_R + V_C$$

$$= L \frac{di(t)}{dt} + i(t) R + y(t).$$

key idea, remove $i(t)$, $di(t)$ and change to $y(t)$.

By $i(t) = C \frac{dy(t)}{dt}$

$$\frac{di(t)}{dt} = C \frac{d^2y(t)}{dt^2}$$

$$\therefore x(t) = L \left(C \frac{d^2y(t)}{dt^2} \right) + C \frac{dy(t)}{dt} R + y(t)$$

now we have a 2nd order eqⁿ based only on $y(t)$.

\hookrightarrow Take Laplace τ .

$$\frac{dy(t)}{dt} \xleftrightarrow{L} sY(s) - y(0)$$

$$\frac{d^2y(t)}{dt^2} \xleftrightarrow{L} s^2Y(s) - sy(0) - \dot{y}(0)$$

of initial conditions of $y(t)$

initial condition of $\dot{y}(t)$

Example: when $X(t) = 10u(t) \xleftrightarrow{\text{Laplace}} \frac{10}{s}$

(ip = unit step.) $y(0) = 0$
 $y'(0) = 0$ | $R=1$
 $L=1$
 $C=\frac{1}{6}$

\therefore substitute into:

$$Y(s) = \left(\frac{1}{s^2 + 1s + 6} \right) \left[\frac{10}{(s)LC} \right] + \underbrace{\text{initial condition}}_{=0}$$

$$= \left[\frac{1}{s^2 + 1s + 6} \right] \left[\frac{10}{\left(\frac{1}{6}s\right)} \right] \quad K(X(t) = Ku(t))$$

$\left(\frac{R}{L}\right) \quad \left(\frac{1}{LC}\right) \quad LC$

$$Y(s) = \frac{10}{\frac{1}{6}s^3 + \frac{1}{6}s^2 + 1s + 0}$$

(PFE) $\Rightarrow r_1 = \begin{bmatrix} -5 + 1.0426j \\ -5 - 1.0426j \\ 0 \end{bmatrix}$

$\leftarrow r_1(1)$
 $\leftarrow r_1(2)$
 $\leftarrow r_1(3)$

$$p_1 = \begin{bmatrix} -0.5 + 2.3979j \\ -0.5 - 2.3979j \\ 0 \end{bmatrix}$$


$\leftarrow p_1(1)$
 $\leftarrow p_1(2)$
 $\leftarrow p_1(3)$

$$K_1 = 0$$

3

$$\therefore y(t) = r_1(1) * \exp(p_1(1) * t) + r_1(2) * \exp(p_1(2) * t) + r_1(3) * \exp(p_1(3) * t)$$

} see Lab-Laplace-Sys-Q4.11.

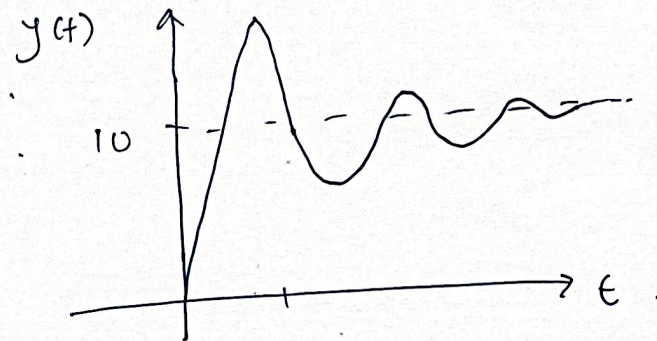

will become 10V at $t \rightarrow \infty$.

using final value theorem.

$$y(t) \rightarrow \infty \Rightarrow sY(s) = \frac{10}{\frac{1}{6}s^2 + \frac{1}{6}s + 1} \Big|_{s \rightarrow 0}$$

$$= \frac{10}{1} = 10V$$